

Direct Current Circuits

No RC circuits, no multiple power supplies


The book is a bit complicated, I'm doing it differently

- * Know how to get the equivalent resistance
- * Think in terms of absolute values

$$|\Delta V| = IR$$


$$P = I\xi = I\Delta V = I^2 R = \frac{\Delta V^2}{R}$$

Ideal Power Supply

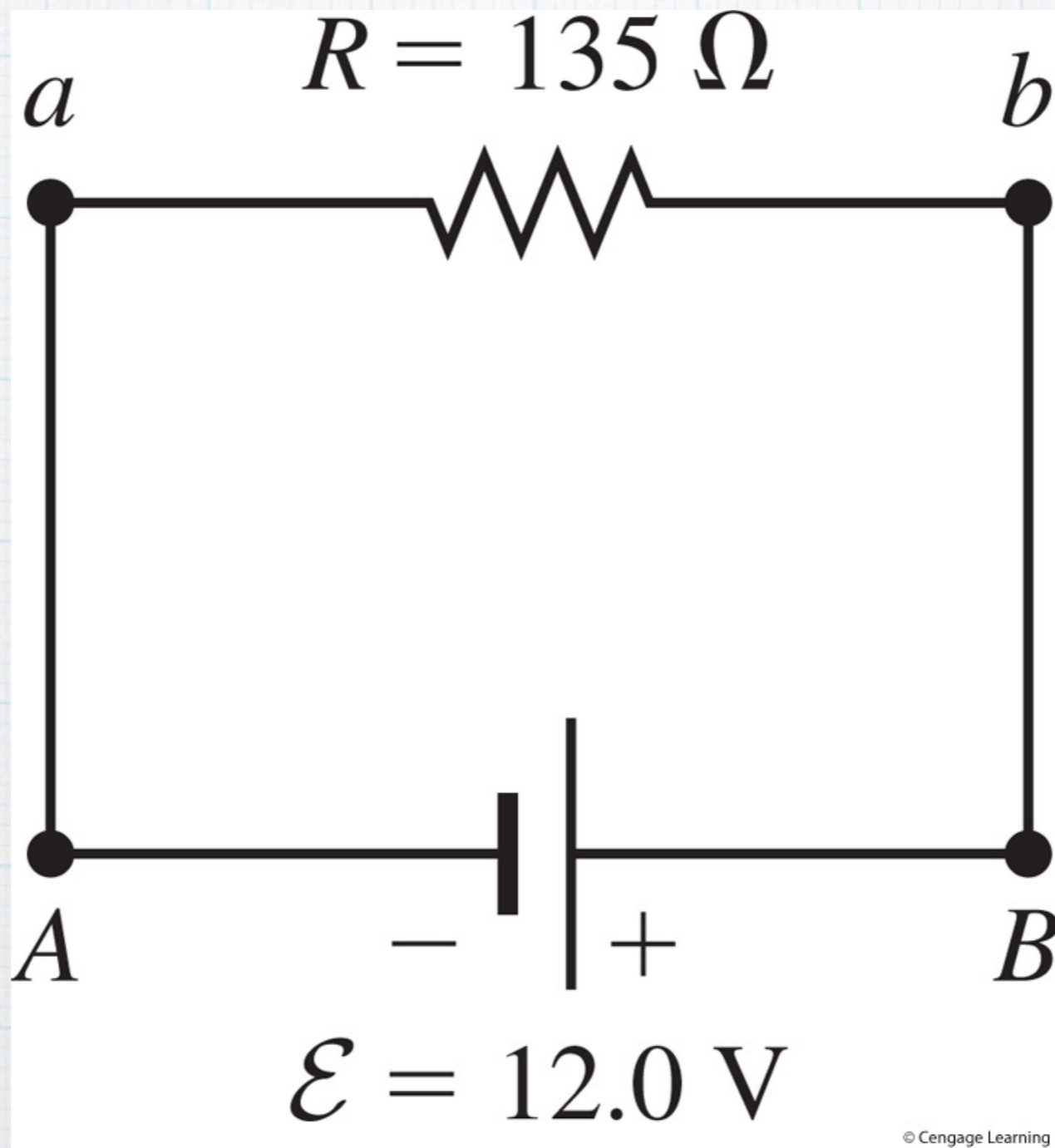

$$|\Delta V| = |IR| = \xi$$

Non-Ideal power supply

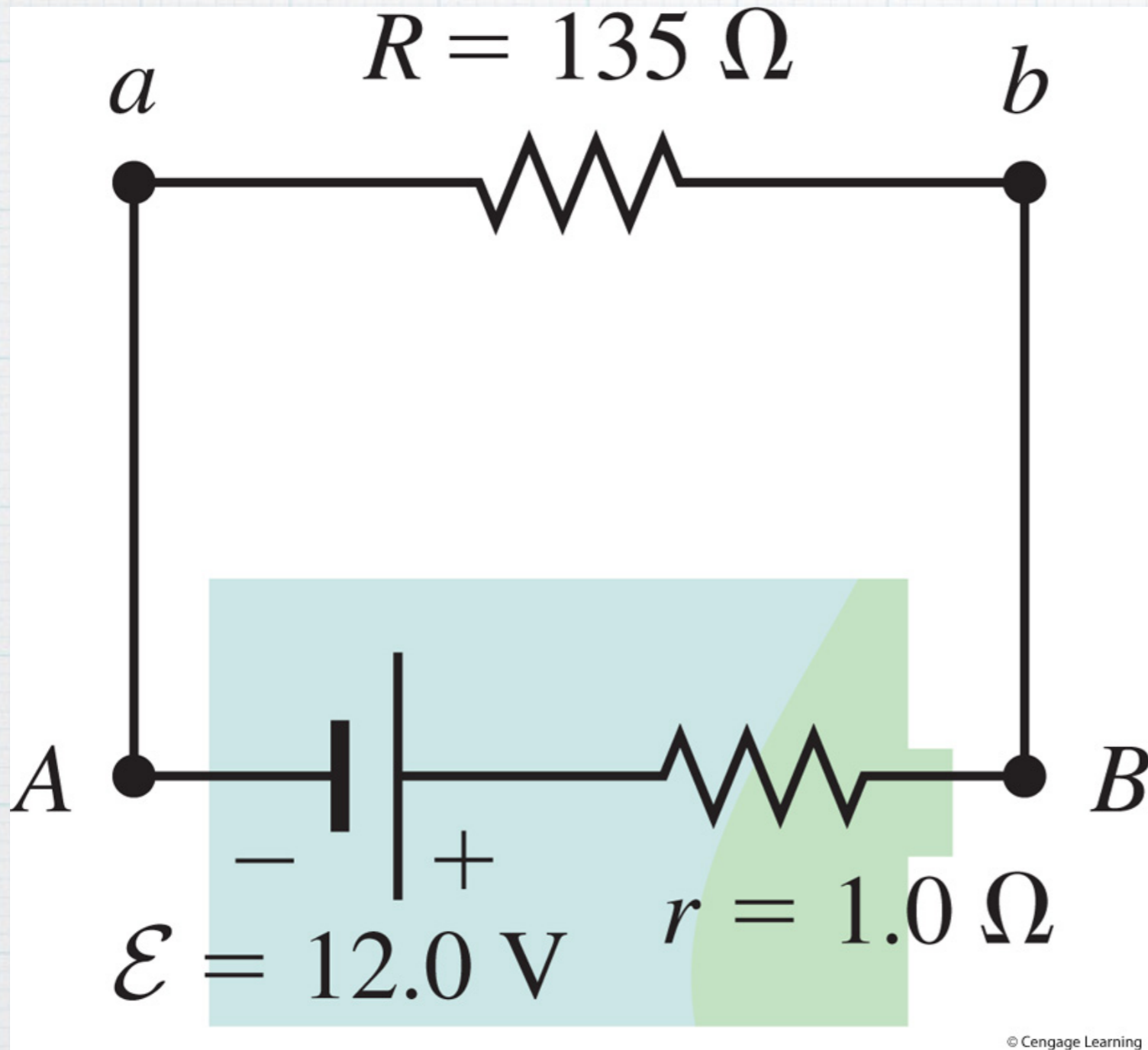

$$|\Delta V| = |Ir| + |IR| = \xi$$

Various Combinations

- * Reduce to one equivalent resistor then work backwards

- * Resistors in series $R_{eq} = \sum_i R_i$


- * Resistors in parallel $\frac{1}{R_{eq}} = \sum_i \frac{1}{R_i}$

- * Waterfall analogy


Rules

- * The current is the same across resistors in series
- * The voltage drop is the same across resistors in parallel
- * Student/door analogy

Series

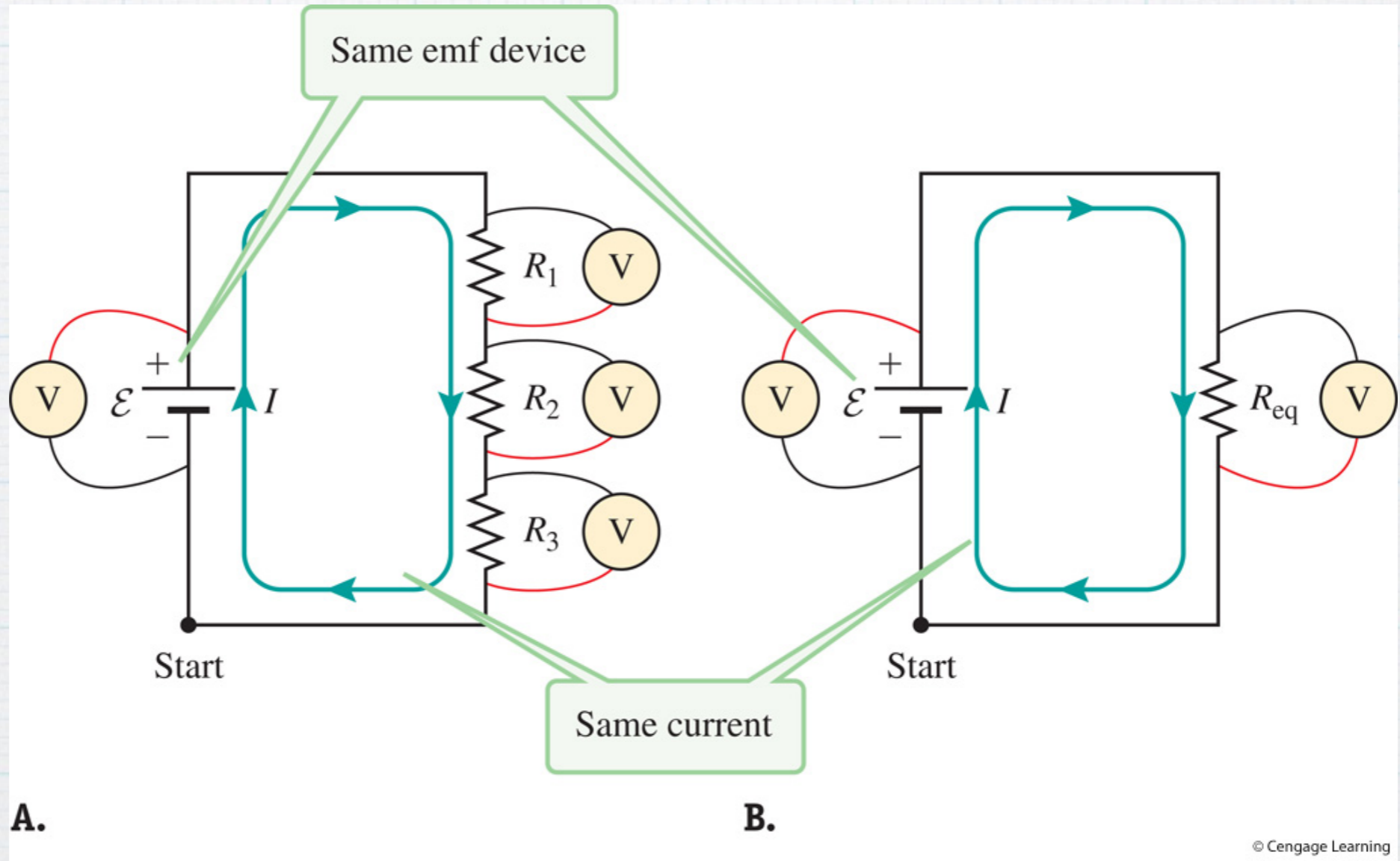

Parallel

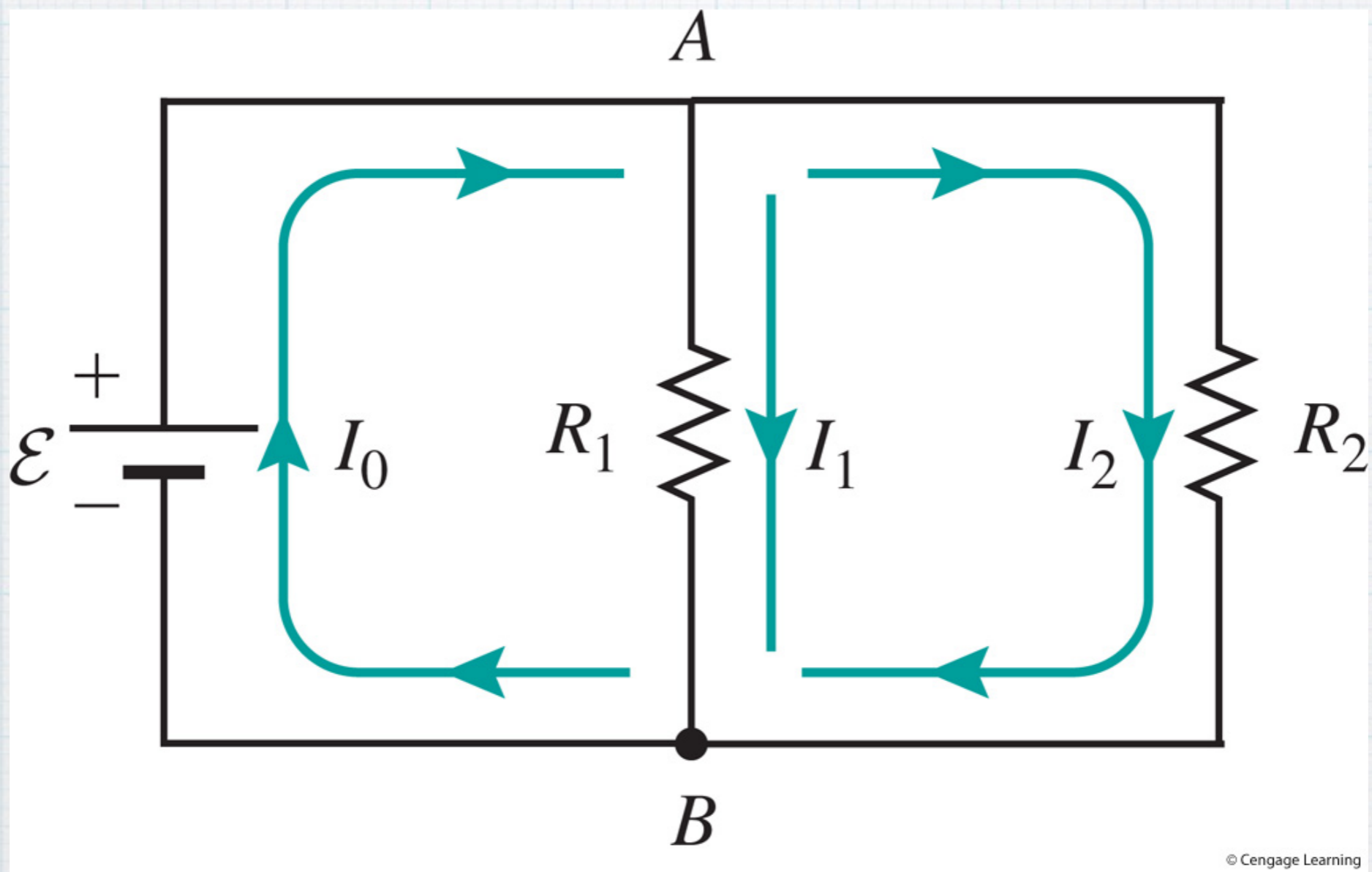

Both

