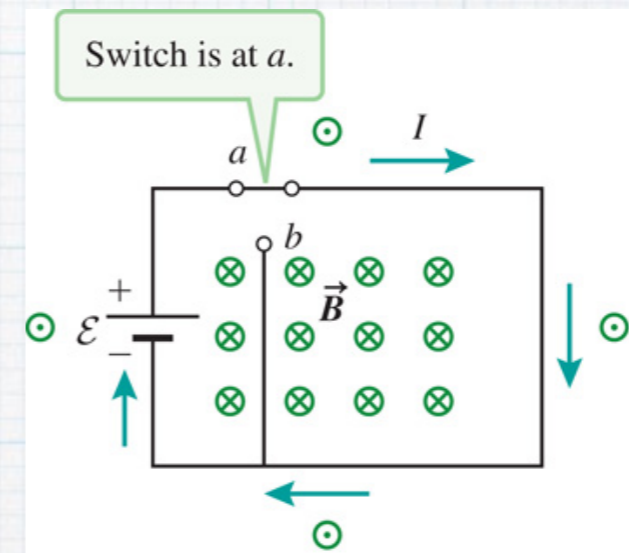



# AC Circuits and Inductors

# Inductors



- \* Circuit element designed to store more magnetic flux and hence more magnetic energy



A.

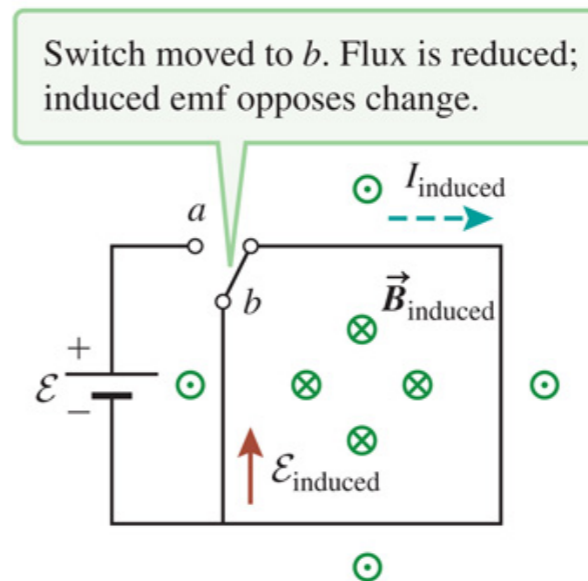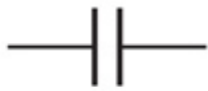

B.

Capacitor			Inductor		
					
$E = \frac{V_C}{d}$	(parallel-plate capacitor)	(27.21)	$B = \mu_0 n I$	(solenoid)	(31.6)
Electric field $E$ between plates			Magnetic field $B$ in coils		
Voltage $V_C$ across plates			Current $I$ in wire		
Charge $Q$ stored by capacitor			Magnetic flux $\Phi_B$ through inductor		
Capacitance $C$			Inductance $L$		
$Q = CV_C$		(27.1)	$\Phi_B = LI$		(33.1)
$C = \frac{\epsilon_0}{d} A$	(parallel-plate capacitor)	(27.10)	$L = \mu_0 n^2 \ell A = \frac{\mu_0 N^2}{\ell} A$	(solenoid)	(33.5)
$U_E = \frac{1}{2} CV_C^2$		(27.3)	$U_B = \frac{1}{2} LI^2$		(33.3)

$$\Phi_t = LI$$

$$1H = 1 \frac{Wb}{A}$$



$$U_B = \frac{1}{2} LI^2$$

$$L \propto A$$

**Inductance of a solenoid**


$$L = \mu_0 n^2 l A$$

**show**

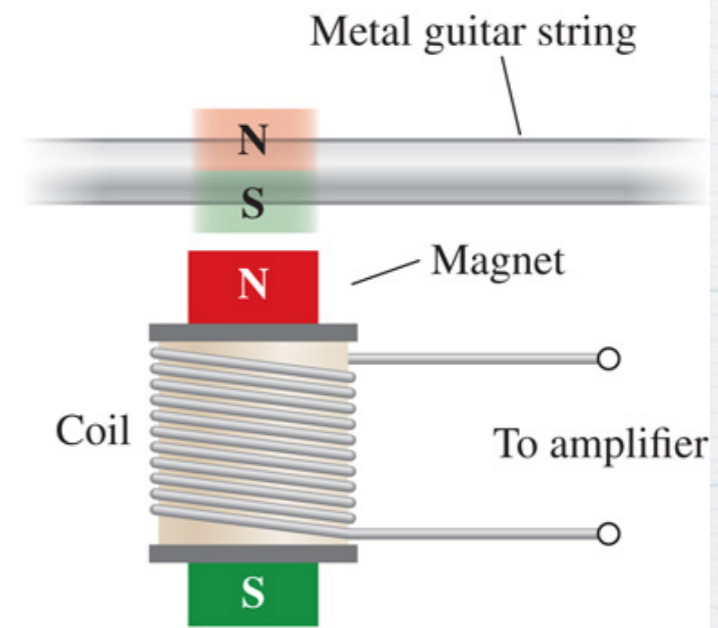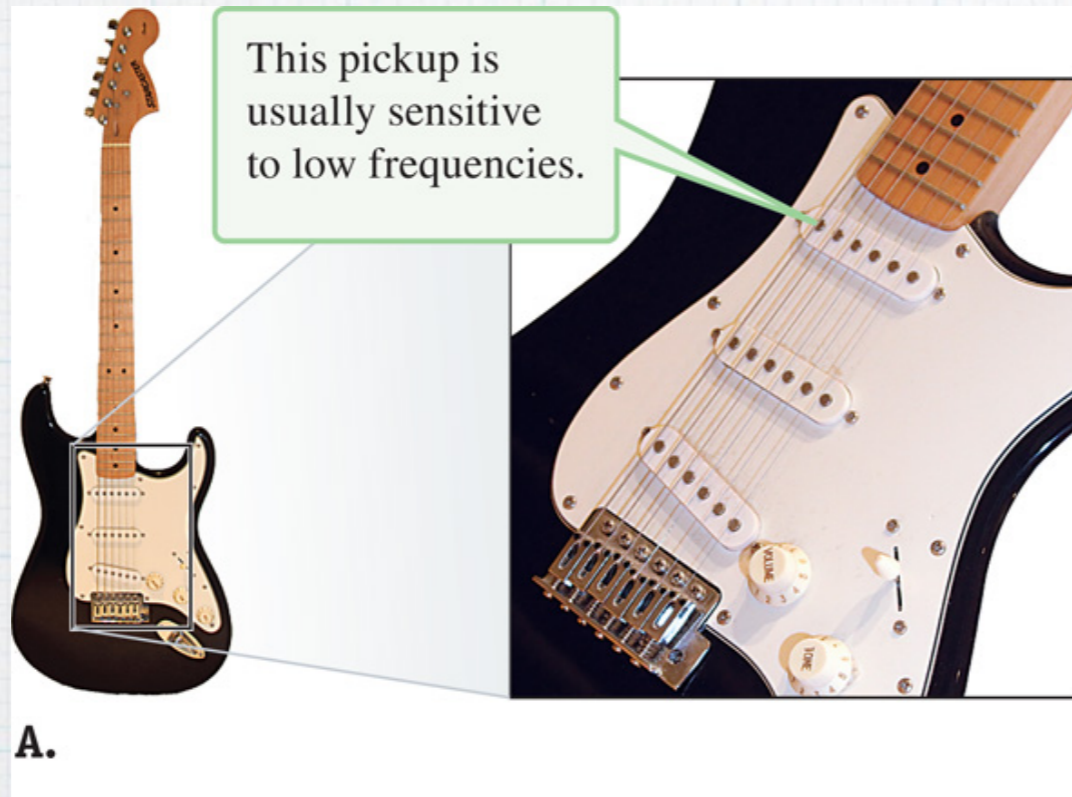


**B.**

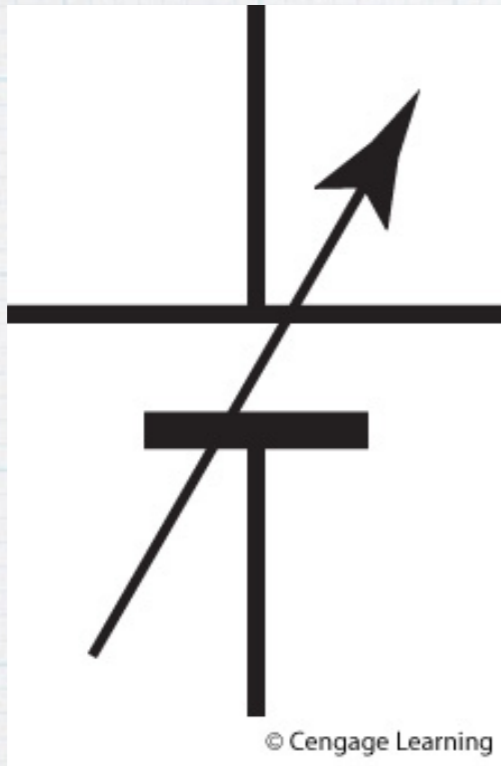a) Peter McGahey/Cengage Learning; b) © Cengage Learning



© Cengage Learning

## Variable DC power supply

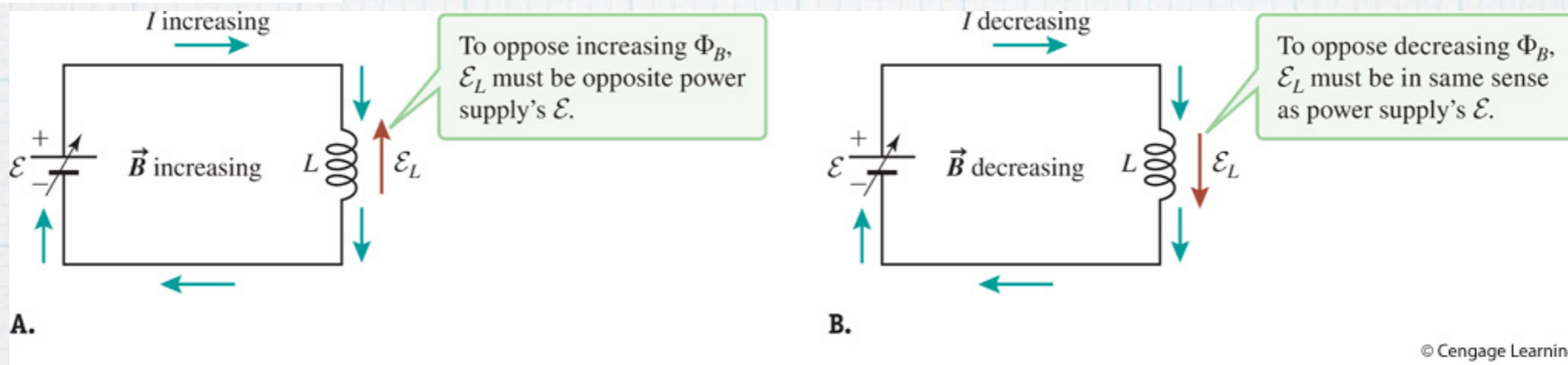

$$\xi_L = \frac{d\Phi}{dt} = L \frac{dI}{dt}$$

**Back EMF**  $\Delta V_L = -L \frac{dI}{dt}$

Depends on what is happening to the current

Example

# Transformers


$$V_p = L \frac{dI}{dt} = N_p \frac{d\Phi_B}{dt}$$

$$V_s = N_s \frac{d\Phi_B}{dt}$$


flux is the same

$$\frac{d\Phi_B}{dt} = \frac{V_s}{N_s} = \frac{V_p}{N_p}$$

Example

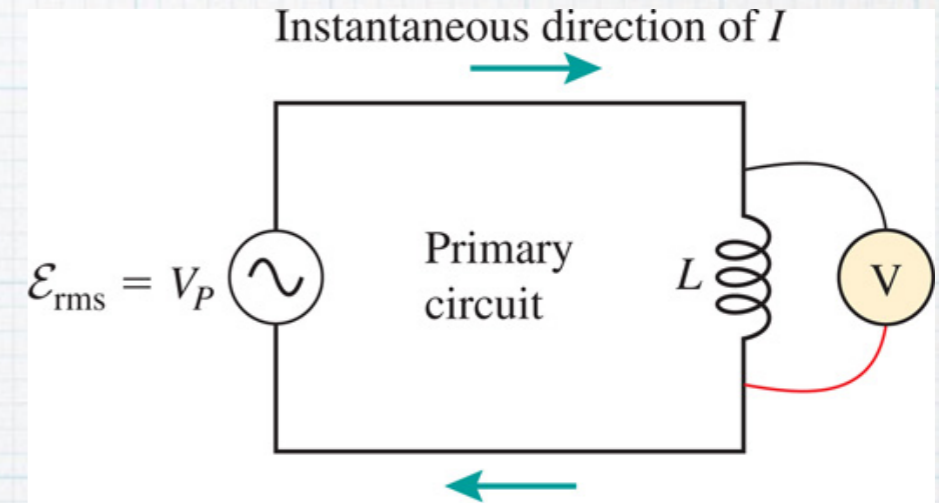


A.

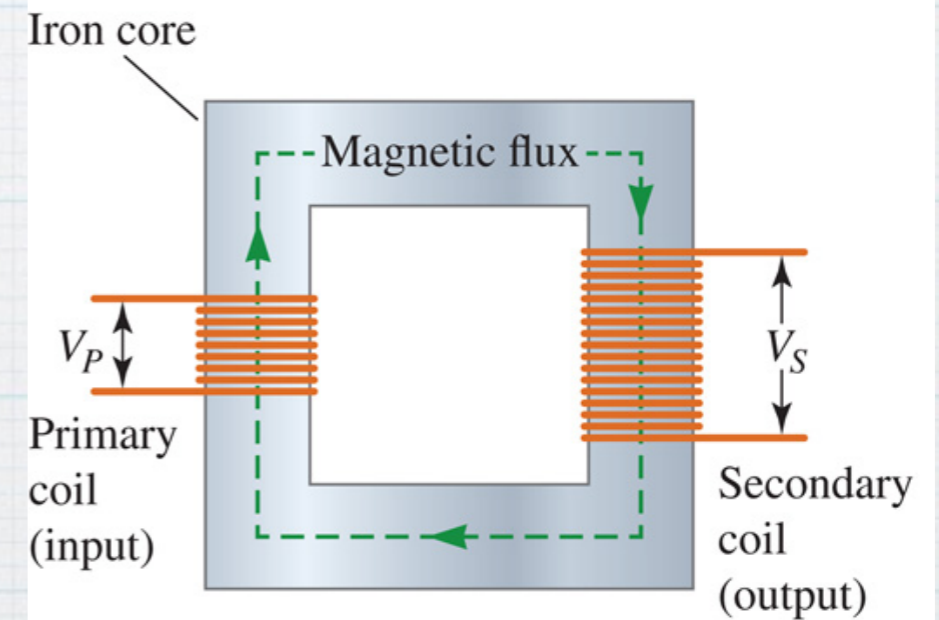

B.



# RL Circuits Power On

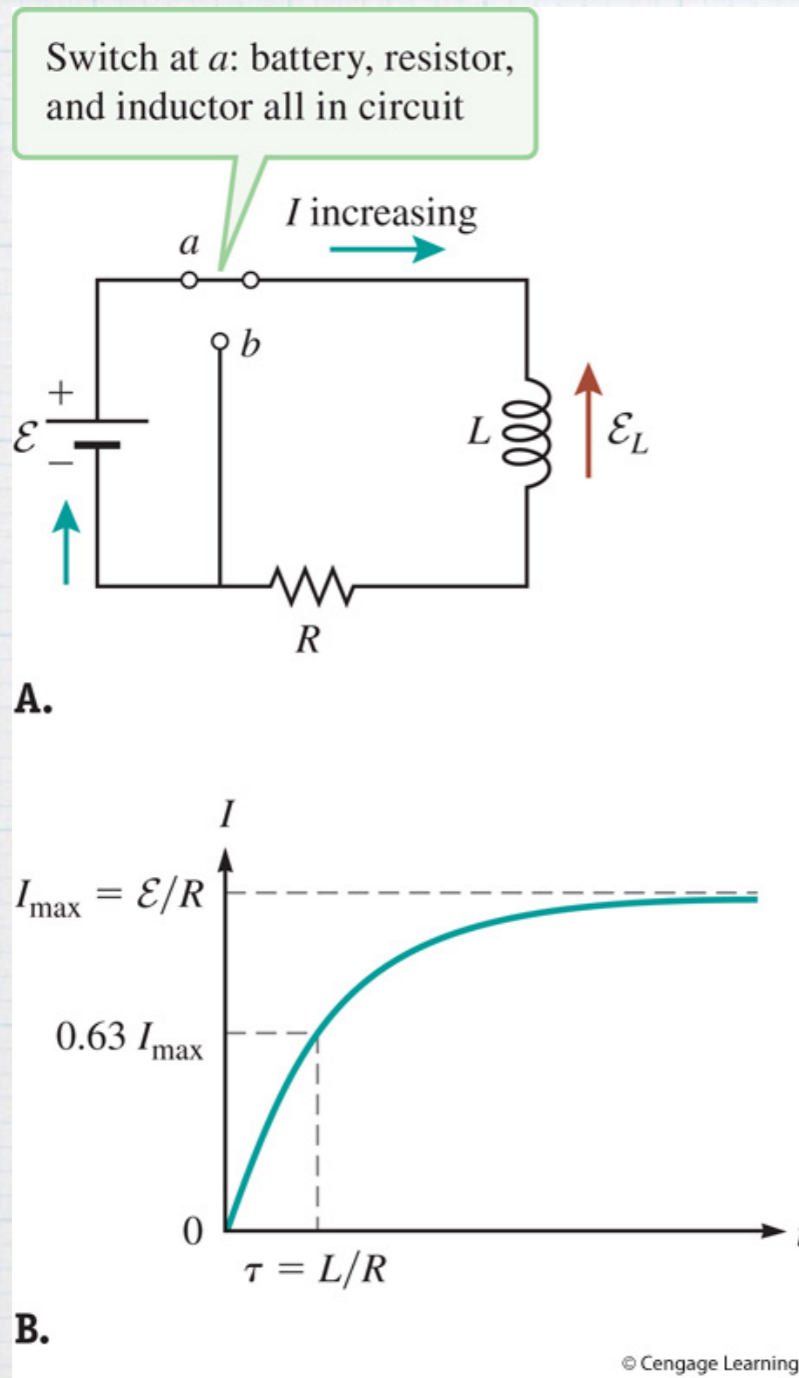

$$\xi - L \frac{dI}{dt} - IR = 0$$

$$\xi - L \frac{d^2q}{dt^2} - \frac{dq}{dt} R = 0$$

$$I(t) = \frac{\xi}{R} (1 - e^{-t/\tau})$$

$$\tau = \frac{L}{R}$$


Example

# RL circuits Power Off

$$L \frac{dI}{dt} + IR = 0$$

$$I(t) = I_{max} e^{-t/\tau}$$

Example

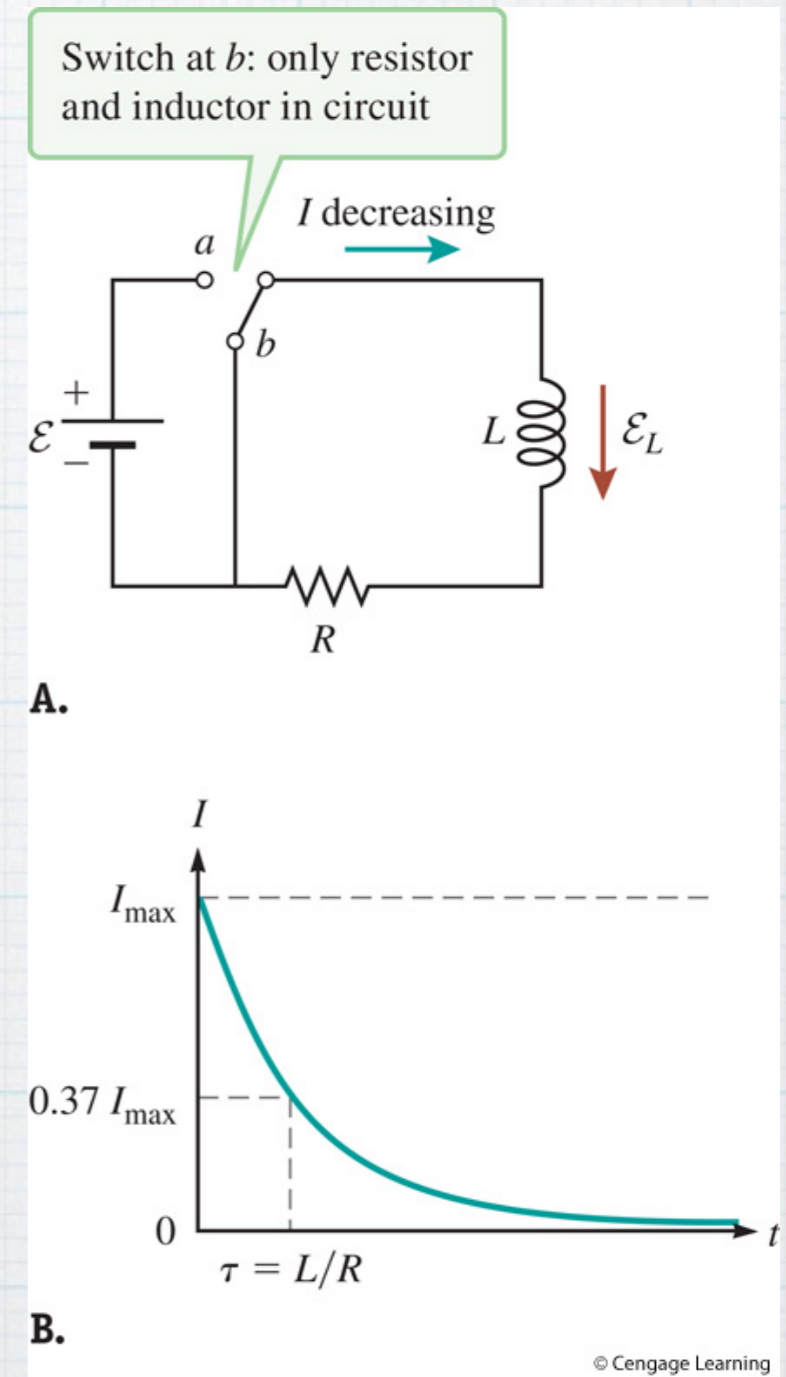

# Energy Stored in the Magnetic Field

$$\xi - L \frac{dI}{dt} - IR = 0$$

Multiply by I, now its a differential equation for power

$$(I\xi)_1 - \left(LI \frac{dI}{dt}\right)_2 - (I^2 R)_3 = 0$$

1: power supply

2: Power stored in inductor

3: power dissipated in resistor

$$\frac{dU_B}{dt} = LI \frac{dI}{dt}$$

# Continued

$$dU_B = LI dI$$

$$\int_0^{U_B} dU_B = L \int_0^I I dI$$

$$U_B = \frac{1}{2} LI^2$$


$$L_{\text{solenoid}} = \mu_0 n^2 l A$$

$$B_{\text{solenoid}} = \mu_0 n I$$

$$U_{B\text{solenoid}} = \frac{1}{2} \frac{B^2}{\mu_0} l A$$
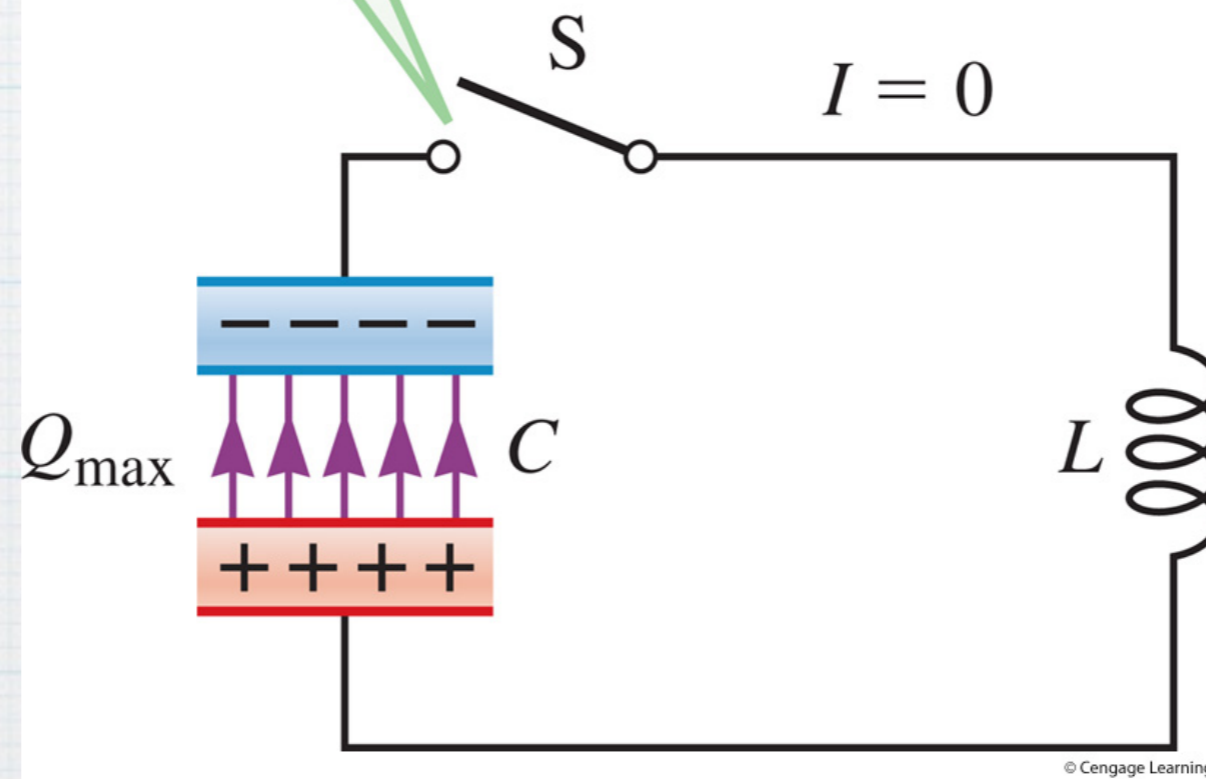
# LC circuit

Capacitor initially fully charged; switch open




$$E_{tot} = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} LI^2 = \frac{1}{2} \frac{Q_{max}^2}{C} = \frac{1}{2} LI_{max}^2 = U_{E,max} = U_{B,max}$$

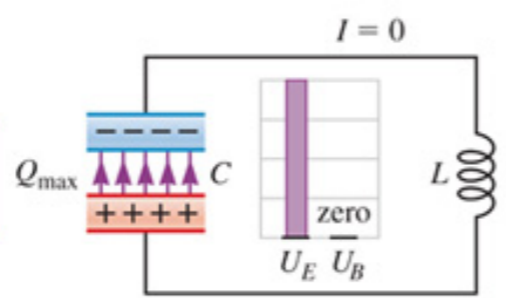
**1 START HERE**

Switch first closed; capacitor charge =  $Q_{max}$ . No current yet; all energy stored in electric field of capacitor.


**9** Circuit returns to initial state and cycle repeats.



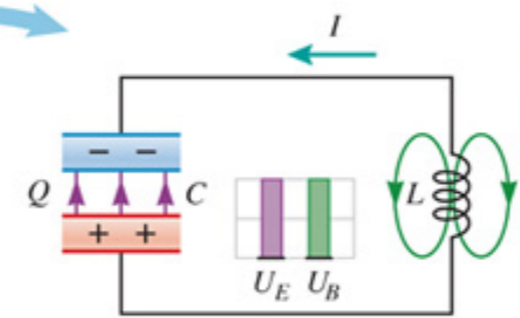
**2** Charge leaves capacitor, producing a current. Some energy in electric field and some in magnetic field of inductor.



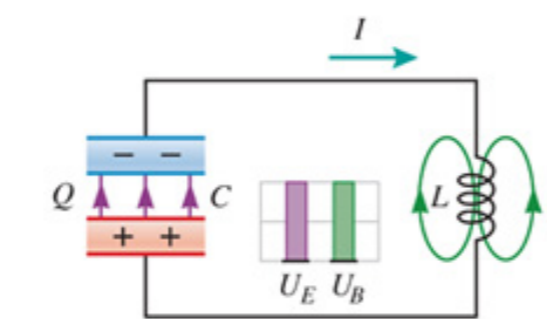
**8** Current in same direction but decreasing. Capacitor charging. Some energy in electric field and some in magnetic field.



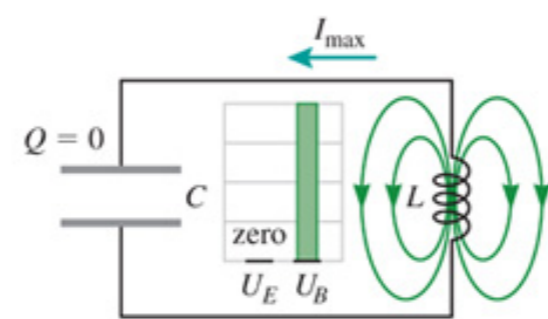
**3** Capacitor completely discharged; maximum current. All energy stored in magnetic field.



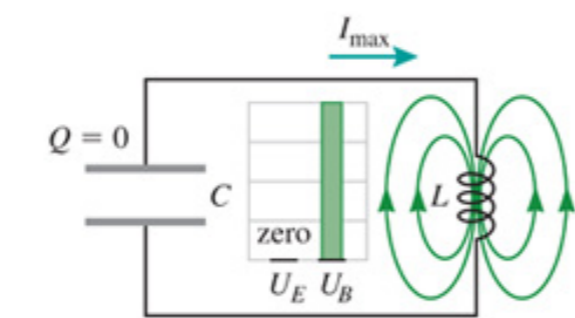
**7** Capacitor completely discharged again; maximum current. All energy in magnetic field.



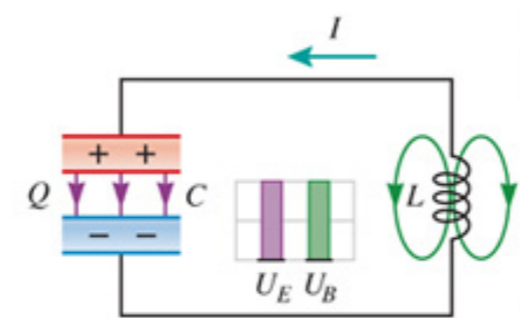
**4** Current in same direction but decreasing. Capacitor charging. Some energy in electric field and some in magnetic field.



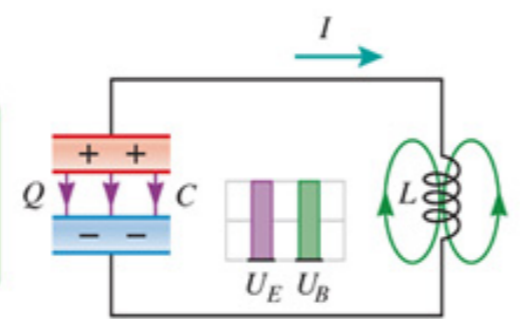**6** Charge leaves capacitor; current in opposite direction. Some energy in electric field and some in magnetic field.



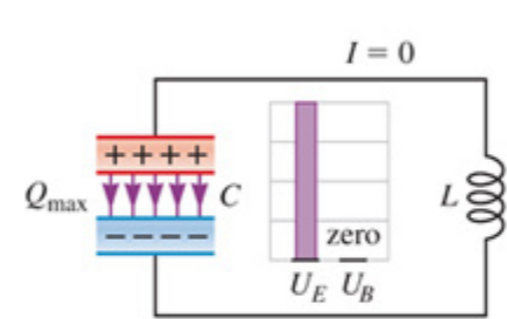**5** Capacitor charge =  $Q_{max}$ ; current momentarily zero. All energy stored in electric field.




# Current and Charge for the LC Circuit

$$Q(t) = Q_{\max} \cos(\omega t + \psi)$$

$$\omega = \sqrt{\frac{1}{LC}}$$

$$I = \frac{dQ}{dt}$$

Example

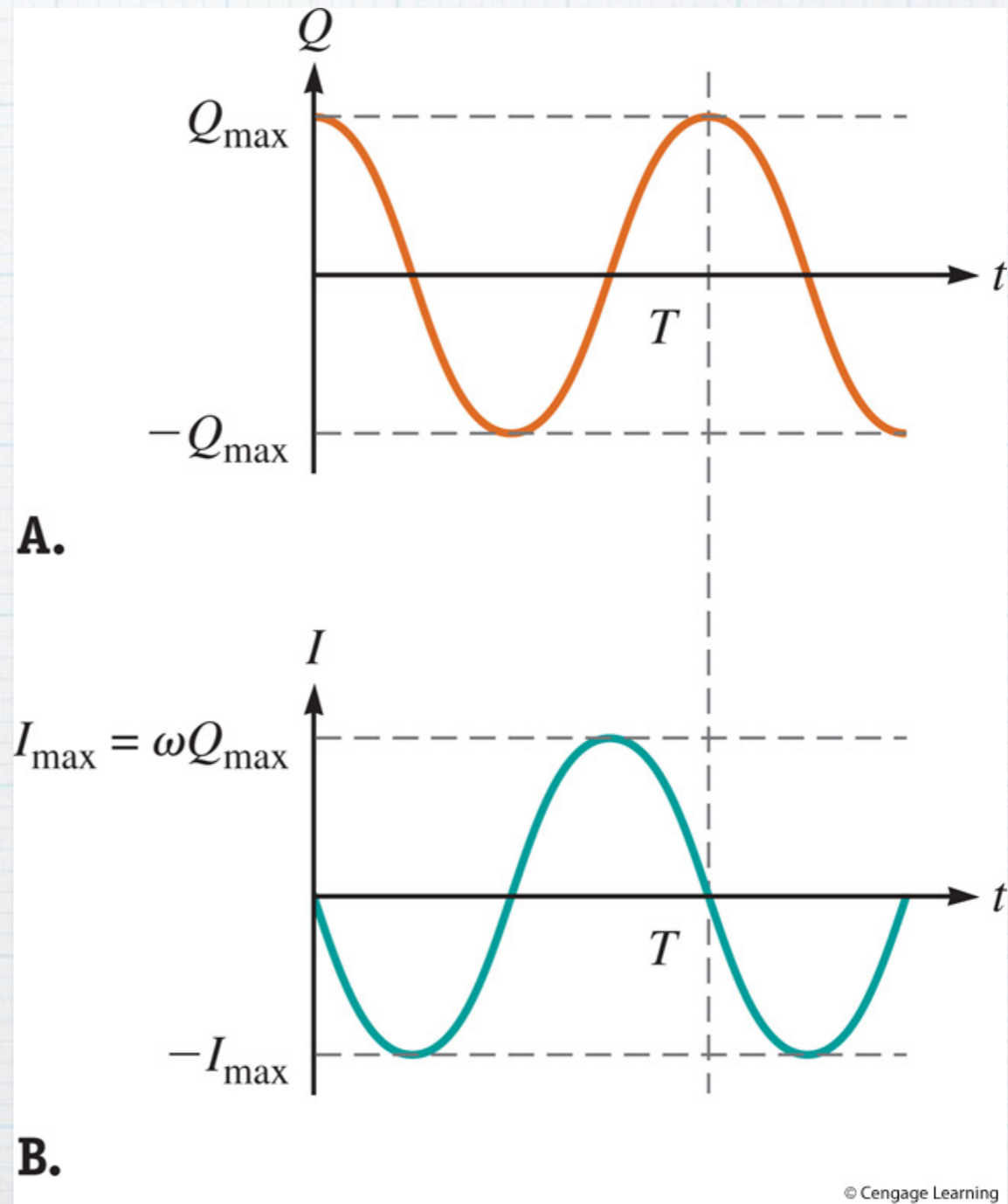


# Energy in an LC Circuit

$$U_E(t) = \frac{Q_{\max}^2}{2C} \cos^2(\omega t + \psi)$$

$$U_B(t) = \frac{Q_{\max}^2}{2C} \sin^2(\omega t + \psi)$$

Show


$$E(t) = U_E + U_B$$

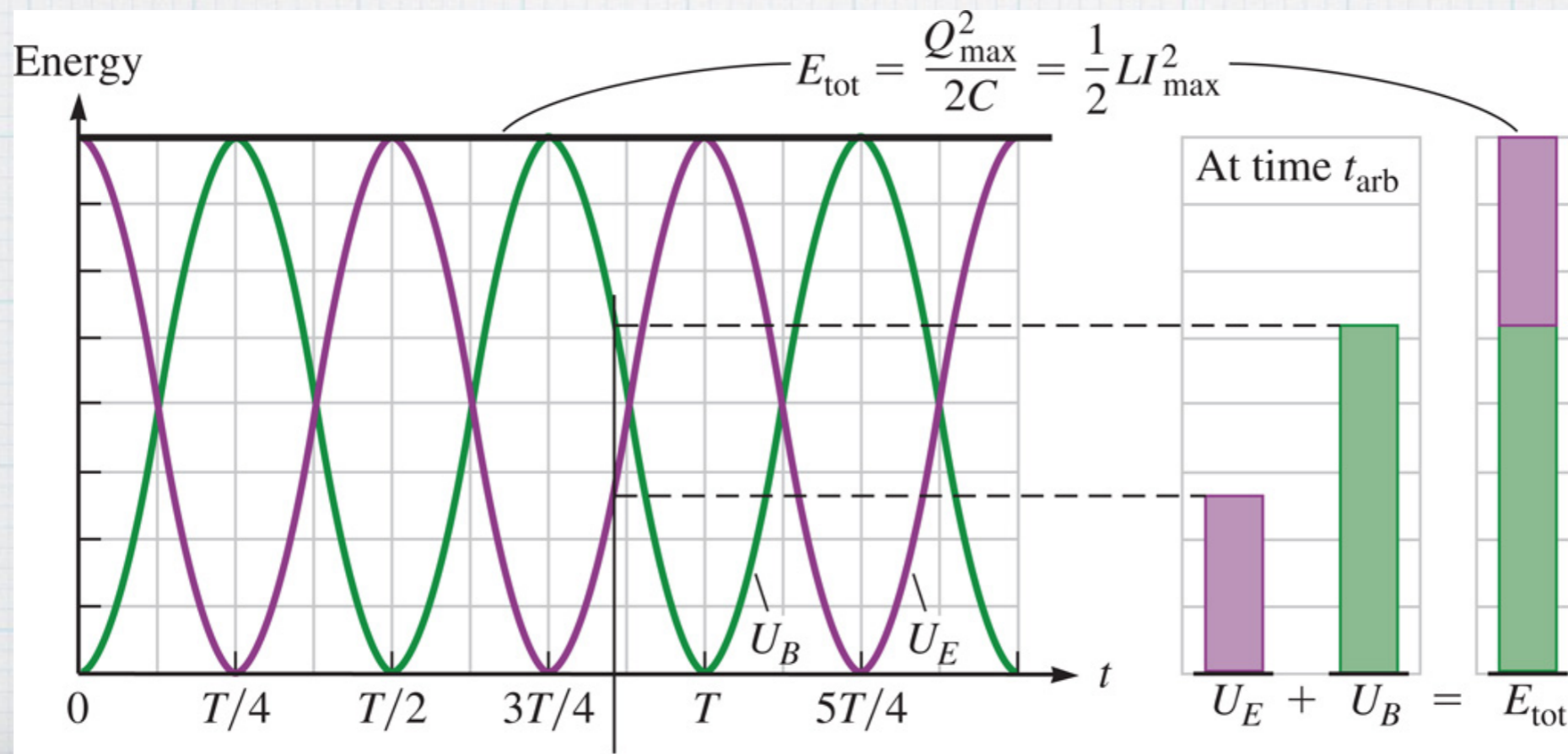






Example

# AC Circuit with Resistance

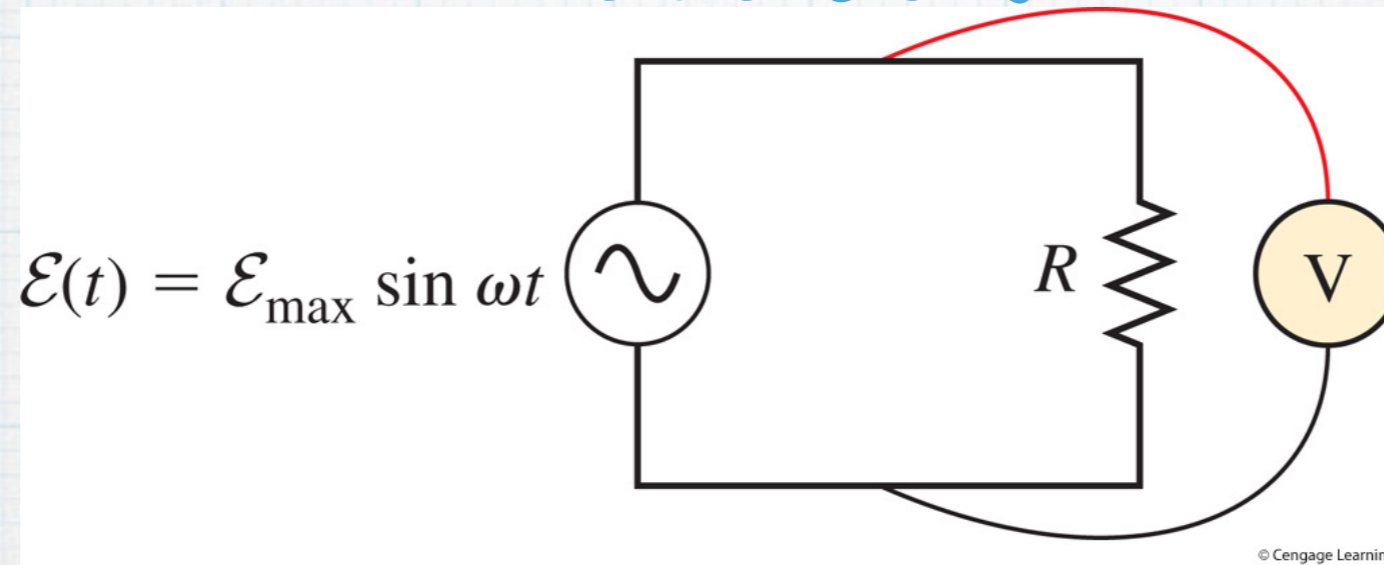


$$V_R(t) = \xi(t) = \xi_{\max} \sin(\omega t)$$

$$I(t) = \frac{\xi(t)}{R}$$

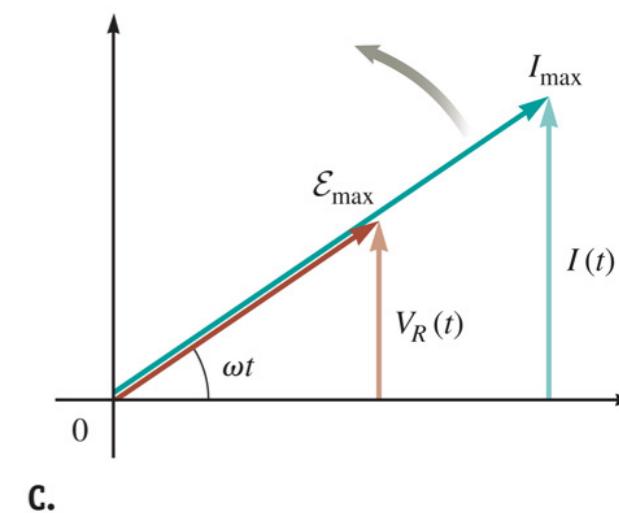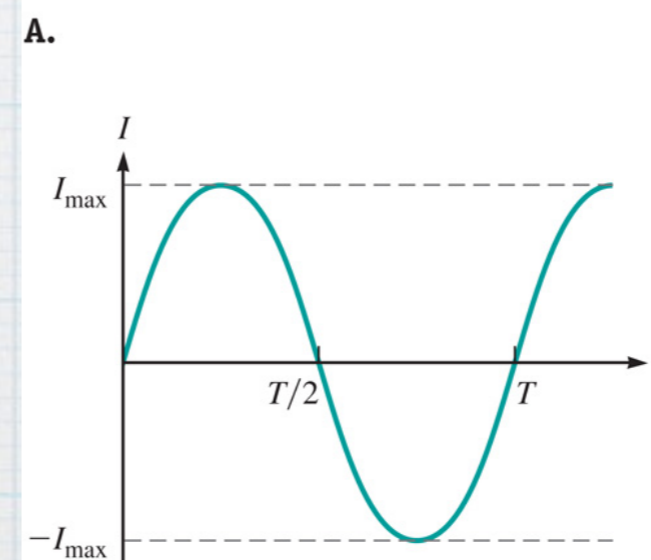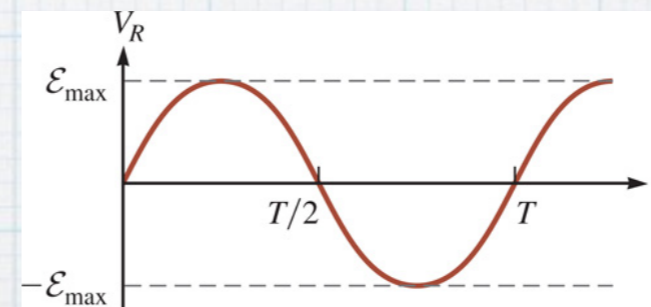


# Example $P(t)$

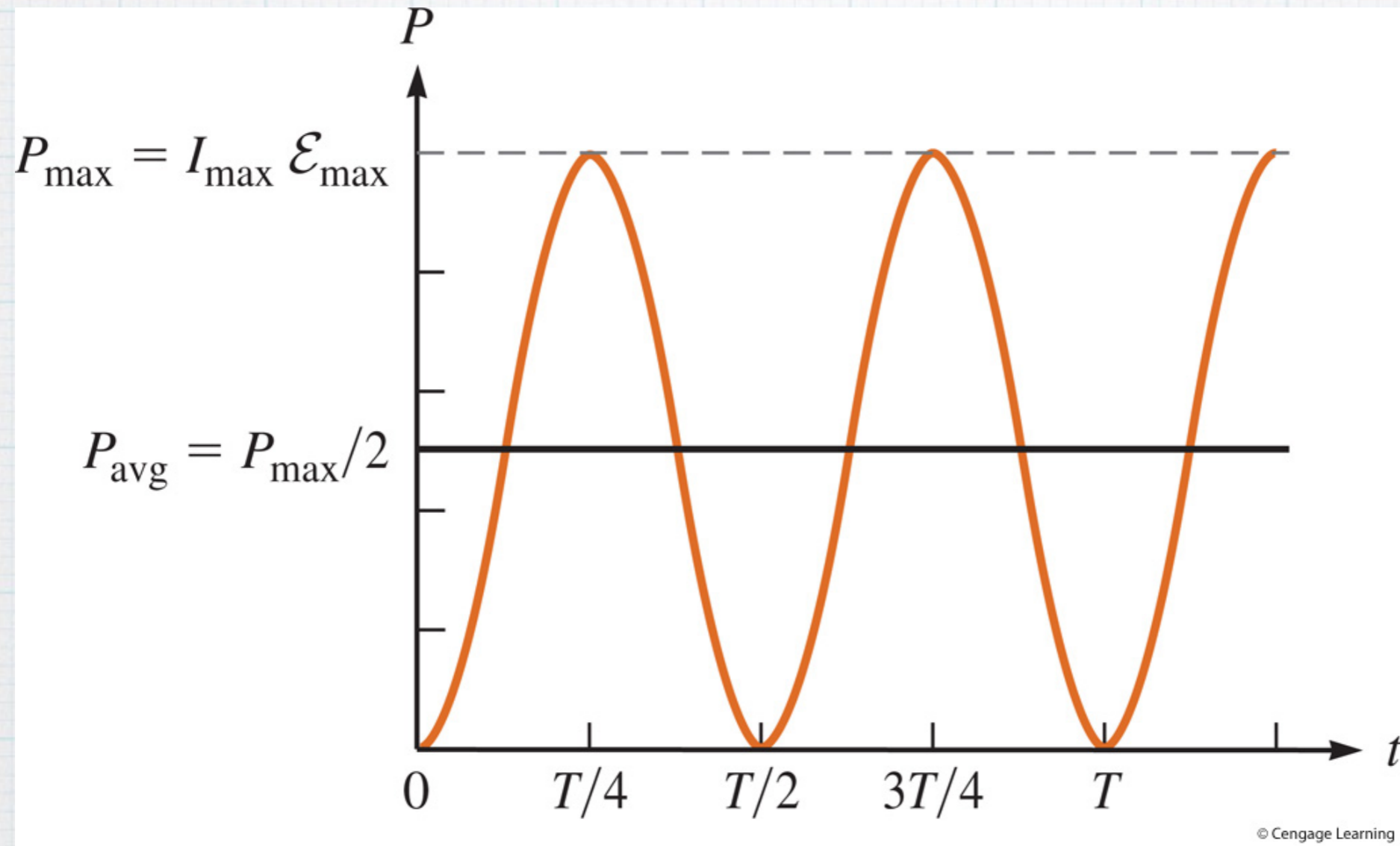

Example

# AC Circuit with Capacitance

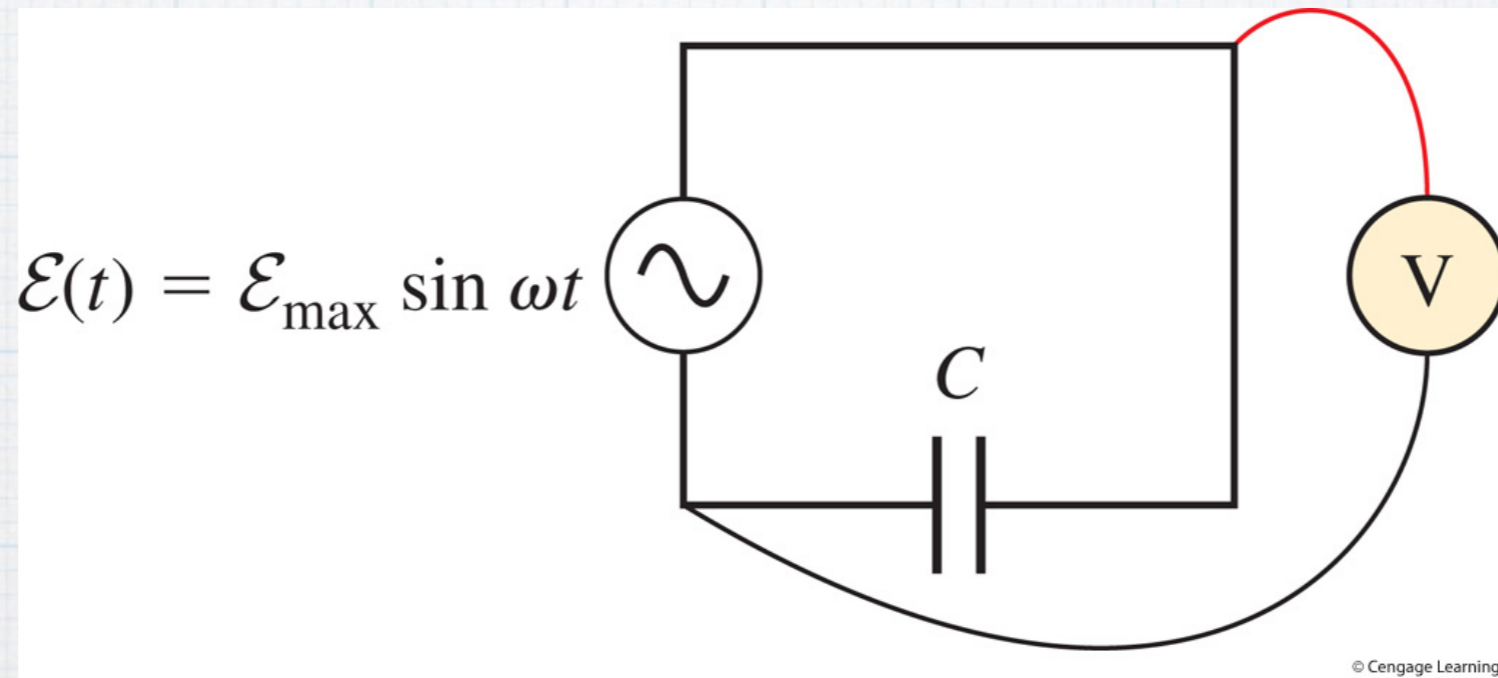

$$V_C(t) = \xi(t) = \xi_{\max} \sin(\omega t)$$



$$Q = CV_C \rightarrow Q(t) = C\xi_{\max} \sin(\omega t)$$

$$I(t) = C\omega\xi_{\max} \cos(\omega t) = C\omega\xi_{\max} \sin(\omega t + 90)$$


$$I(t) = \frac{\xi_{max}}{X_C} \sin(\omega t + 90)$$

$$X_C = \frac{1}{\omega C}$$

## capacitive reactance

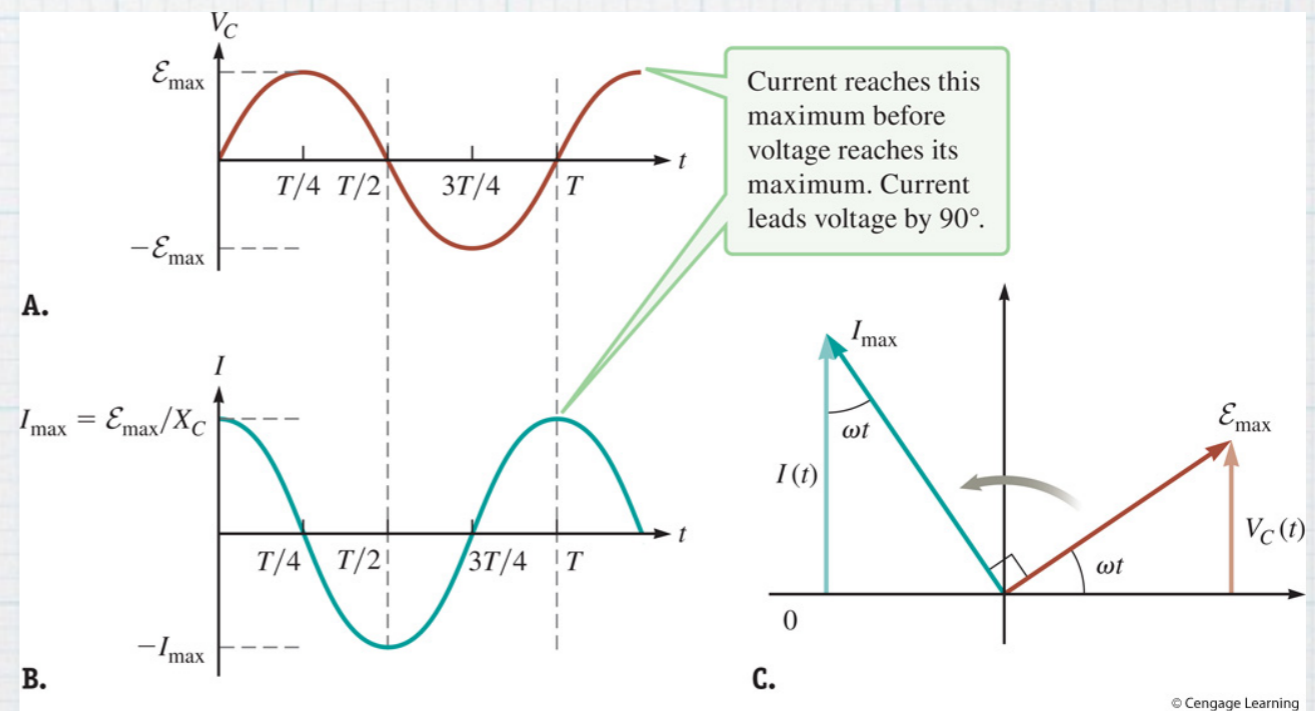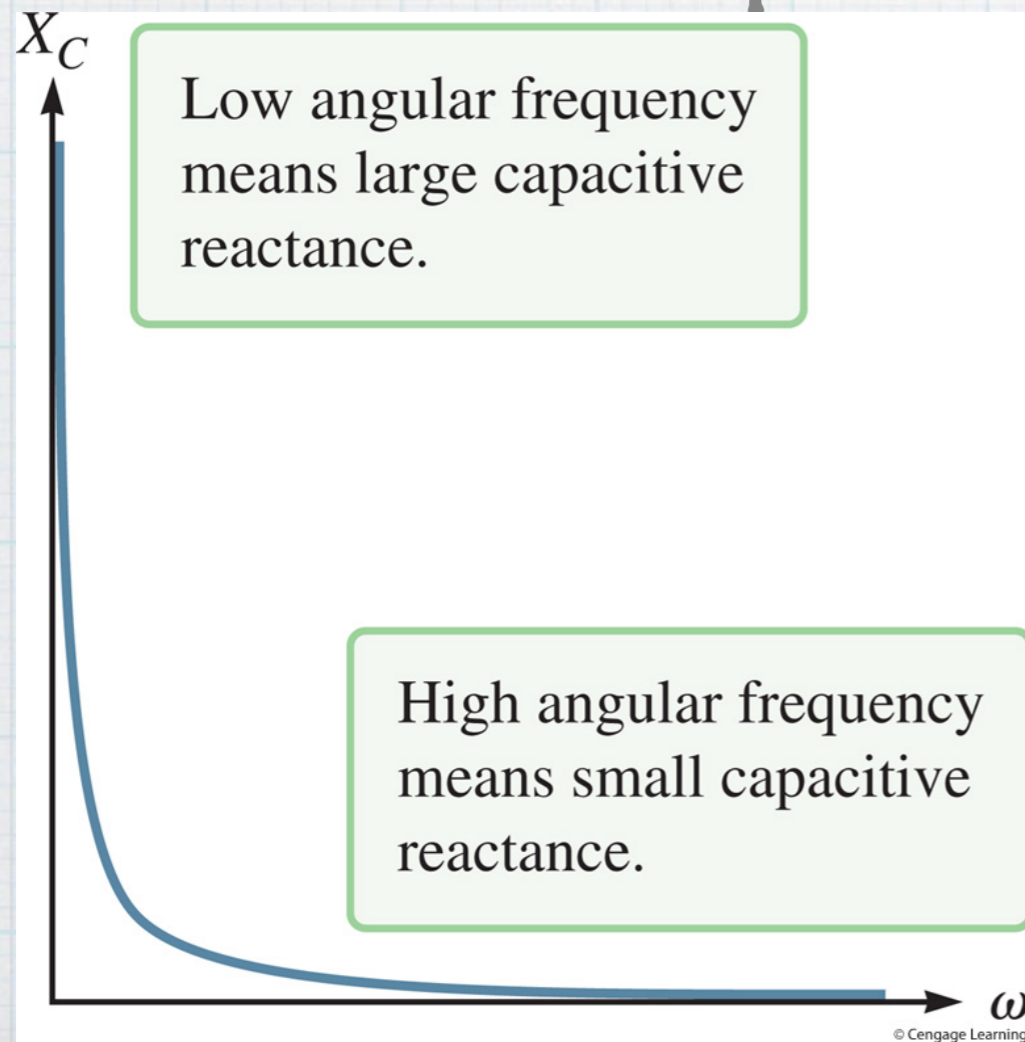


# Example, power in AC circuits

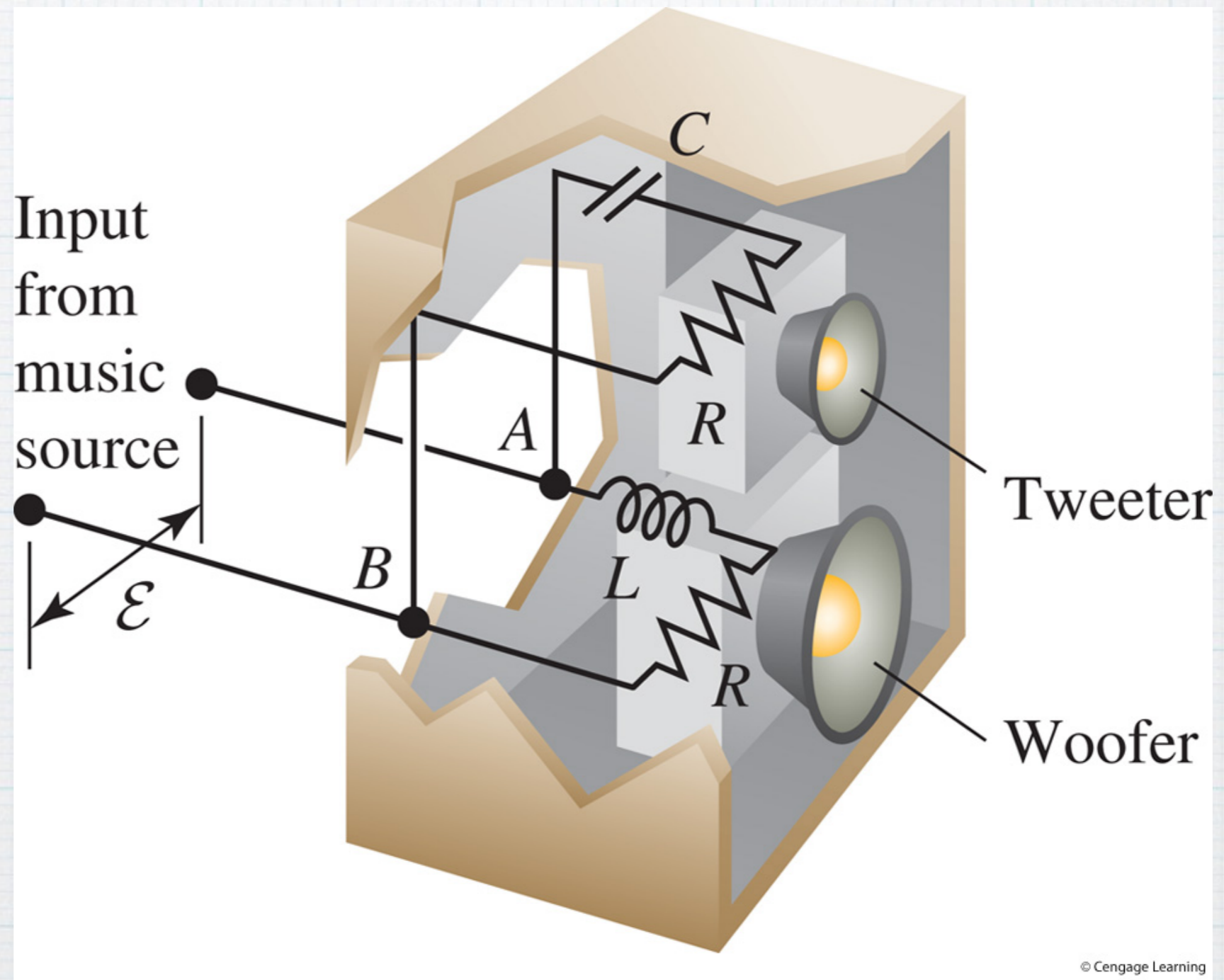




# RC Filters

No derivations

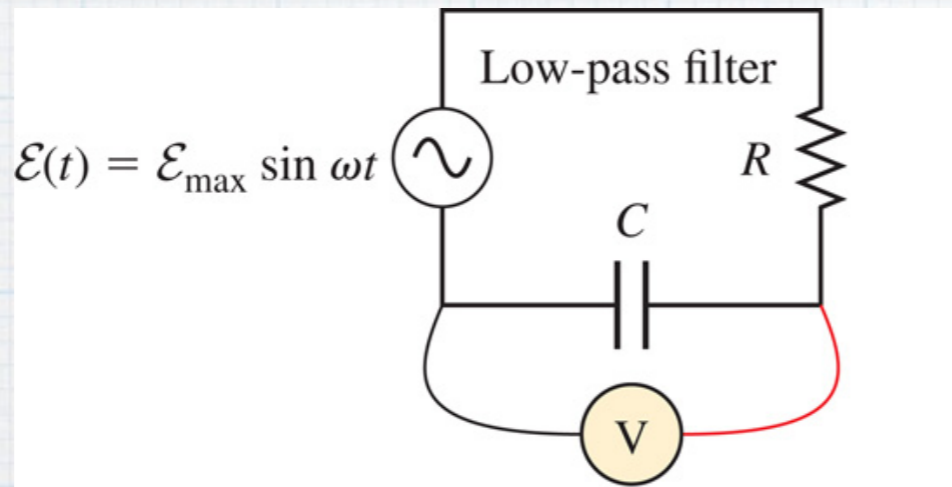

A.

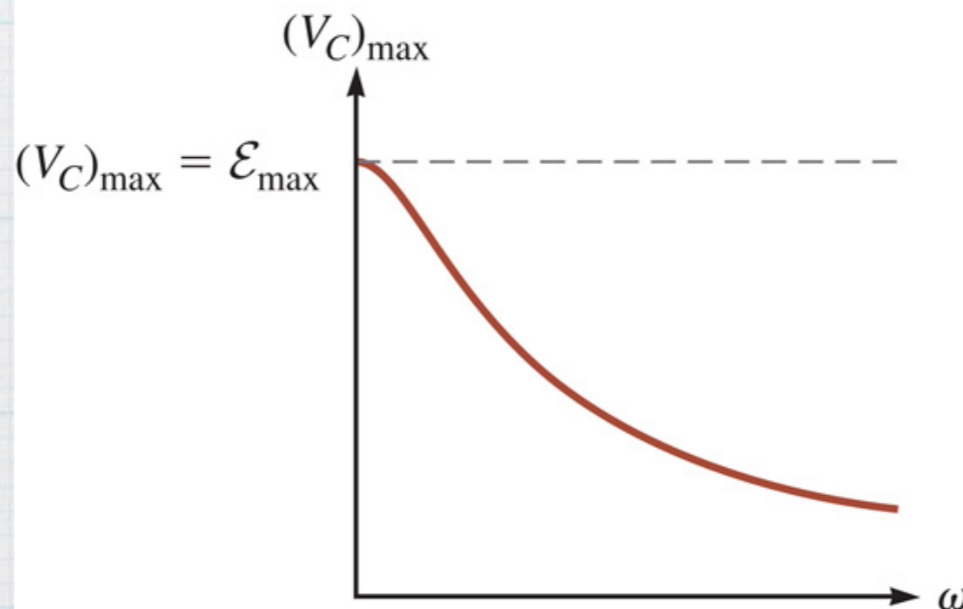

B.


$$V_C(T) = X_C I_{\max} \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$I_{\max} = \frac{\xi_{\max}}{\sqrt{X_C^2 + R^2}}$$


$$V_{C,\max} = X_C I$$

woofer

# RC Filters

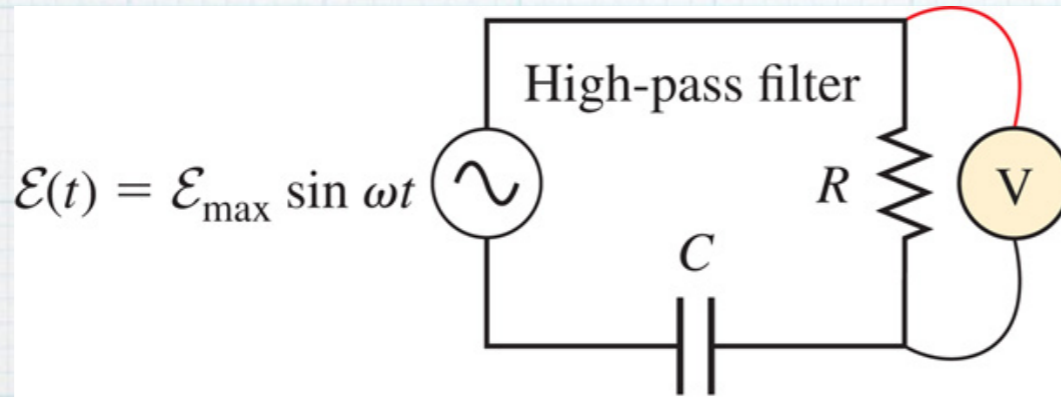

A.

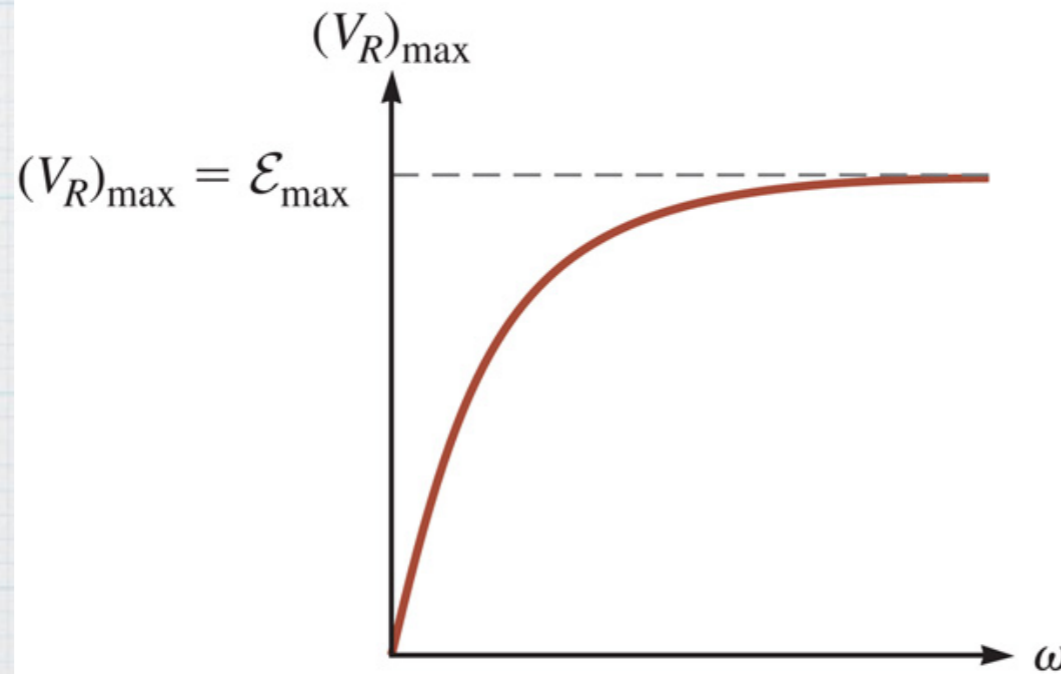

B.

$$V_R(t) = RI_{\max} \sin(\omega t)$$

$$I_{\max} = \frac{\mathcal{E}_{\max}}{\sqrt{X_C^2 + R^2}}$$

$$V_{R,\max} = RI_{\max}$$

tweeter

Example